



Tutorial _1

- 1- Simplify the following Boolean expressions to a minimum number of literals:
 - a. $ABC + A'B + ABC'$
 - b. $x'yz + xz$
 - c. $(x + y)'(x' + y')$
 - d. $xy + x(wz + wz')$

- 2- Draw the logic diagram of the circuits that implement the original and the simplified expression in problem 1

- 3- Reduce the following Boolean expressions to the indicated number of literals:
 - a. $A'C' + ABC + AC'$ to three literals
 - b. $(x'y' + z)' + z + xy + wz$ to three literals
 - c. $A'B(D' + C'D) + B(A + A'CD)$ to one literal
- 4- For the Boolean function
$$F = xy'z + x'y'z + w'xy + wx'y + wxy$$
 - a. Obtain the truth table of F.
 - b. Draw the logic diagram. using the original Boolean expression.
 - c. Use Boolean algebra to simplify the function to a minimum number of literals,
 - d. Obtain the truth table of the function from the simplified expression and show that it is the same as in part a.

- 5- Convert each of the following to the other canonical form:
 - a. $F(x,y,z) = \Sigma(2,5,6)$
 - b. $F(A,B,C,D) = \Pi(0,1,2,4,7,9,12)$



- 6- Express the following function as a sum of minterms and as a product of maxterms:

$$F(A, B, C, D) = B'D + A'D + BD$$

- 7- Simplify the following Boolean functions. using four-variable maps (use K-map):

- $F(w, x, y, z) = \Sigma (1, 4, 5, 6, 12, 14, 15)$
- $F(A, B, C, D) = \Sigma (1, 5, 9, 10, 11, 14, 15)$
- $F(w, x, y, z) = \Sigma (0, 1, 4, 5, 6, 7, 8, 9)$

- 8- Simplify the following Boolean expressions, using three-variable maps (use K-map):

- $F(x, y, z) = xy + x'y'z' + x'y'z'$
- $F(x, y, z) = x'y' + yz + x'yz'$
- $F(x, y, z) = x'y + yz' + y'z'$

- 9- Simplify the following Boolean functions to product-of-sums form(use K-map):

- $F(w, x, y, z) = \Sigma (0, 1, 2, 5, 8, 10, 13)$
- $F(A, B, C, D) = \Pi (1, 3, 5, 7, 13, 15)$
- $F(A, B, C, D) = \Pi (1, 3, 6, 9, 11, 12, 14)$

- 10- Design a combinational circuit with three input and one output.
- The output is 1 when the binary value of the inputs is less than 3. the output is 0 otherwise.
 - The output is 1 when the binary value of the input is an odd number.



- 11- A majority circuit is a combinational circuit whose output is equal to 1 if the input variables have more 1's than 0's. The output is 0 otherwise.
- Design a three inputs majority circuit by finding the circuits truth table. Boolean equation and a logic diagram.

- 12- Design an Excess-3 to binary decoder using the unused combinations of the code as don't care conditions.

- 13- Construct a 5-to 32 line decoder with four 3 -to-8- line decoders with enable and a 2-to-4 line decoder. Use block diagrams for the components.

- 14- Construct a 4-to-16 line decoder with 2-to-4 line decoders with enable.

- 15- A combinational circuit is specified by the following three Boolean functions:

- $F1(A,B,C) = \Sigma(3,5,6)$
- $F2(A,B,C) = \Sigma(1,4)$
- $F2(A,B,C) = \Sigma(2,3,5,6,7)$

Implement the circuit with decoder constructed with NAND gates and NAND gates connected to the decoder outputs. Use a block diagram for the decoder.

- 16- An 8 X 1 multiplexer has inputs A, B, and C connected to the selection inputs S_2 , S_1 and S_0 , respectively. The data inputs I_0 through I_7 are as follows:

- $I_1 = I_2 = I_7 = 0$; $I_3 = I_5 = 1$; $I_0 = I_4 = D$; and $I_6 = D'$.
- $I_1 = I_2 = 0$; $I_3 = I_7 = 1$; $I_4 = I_5 = D$; and $I_0 = I_6 = D'$.



17- Implement the following Boolean function with a 4 X 1 multiplexer and external gates.

a. $F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$

b. $F(A, B, C, D) = \Sigma(1, 2, 4, 7, 8, 9, 10, 11, 13, 15)$

Connect Inputs A and B to the selection lines. The input requirements for the four data lines will be a function of variables C and D. These values are obtained by expressing F as a function of C and D for each of the four cases when AB = 00, 01, 10, and 11. The functions may have to be implemented with external gates and with connections to power (1) and ground (0).